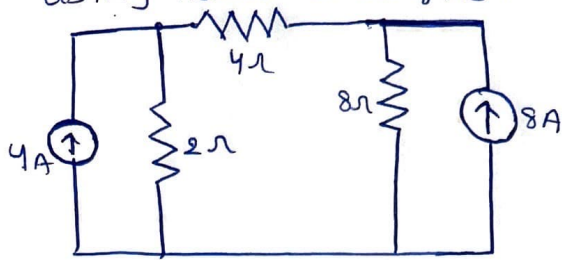
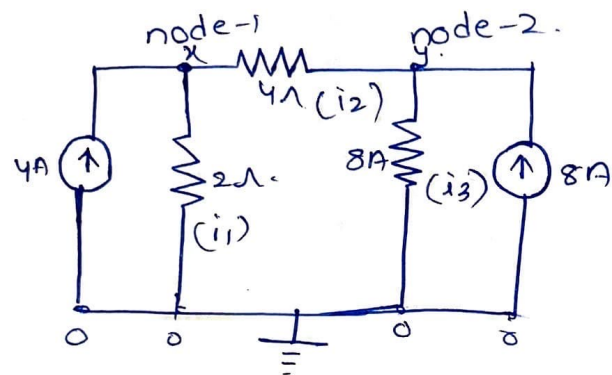


1) Find the current flowing through various resistors using nodal analysis.



Sol:-

1st let's consider nodes and assume node voltages.



Applying nodal analysis at node-1

$$\frac{x-0}{2} + \frac{x-y}{4} = 4$$

$$2x + x - y = 4 \times 4$$

$$3x - y = 16 \quad \text{--- (1)}$$

Applying nodal analysis at node-2

$$\frac{y-0}{8} + \frac{y-x}{4} = 8$$

$$2y - 2x + y = 64$$

$$3y - 2x = 64 \quad \text{--- (2)}$$

on solving equation (1) and eqn (2) we get.

$$x = 16 \text{ V}$$

$$y = 32 \text{ V}$$

current through resistors

$$i_1 = \frac{x-0}{2} = \frac{16}{2} = 8 \text{ A}$$

$$i_2 = \frac{x-y}{4} = \frac{16-32}{4} = -4 \text{ A}$$

$$i_3 = \frac{y-0}{8} = \frac{32}{8} = 4 \text{ A}$$